



Electric Power Systems (2)

Please Answer The Following Questions:

Question # 1: (20 Mark)

For the power system shown in Fig.1, the data of various system components are as follows:

G: 30 MVA, 11 kV, $X = 0.3$ p.u.

T1: 30 MVA, 11/33 kV, $X = 5 \Omega$ /phase referred to low voltage side.

T2: 25 MVA, 33/6.6 kV, $X = 12 \Omega$ /phase referred to high voltage side.

Line: $Z = 4 + j20$ ohms/phase.

Load: $S = 6 + j4$ MVA, 6.6 kV.

- a- Draw the impedance diagram with all values on per unit (Base 30 MVA and 6.6 kV in load side).
- b- Calculate the generator voltage and generator output power under loading conditions.
- c- Voltage regulation of the system.

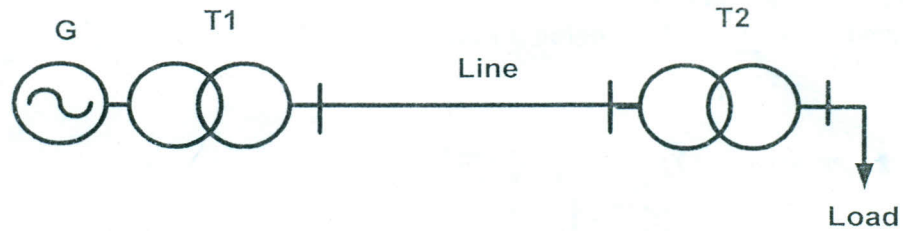


Fig. 1

Question # 2: (15 Mark)

For the power system given in figure 2, a 3-phase to ground fault occurs at the motor terminal, neglecting the pre-fault load current find:

- (i) Subtransient fault current in kA.
- (ii) Voltage of bus 1 in kV.
- (iii) Momentary current of breaker A in kA.

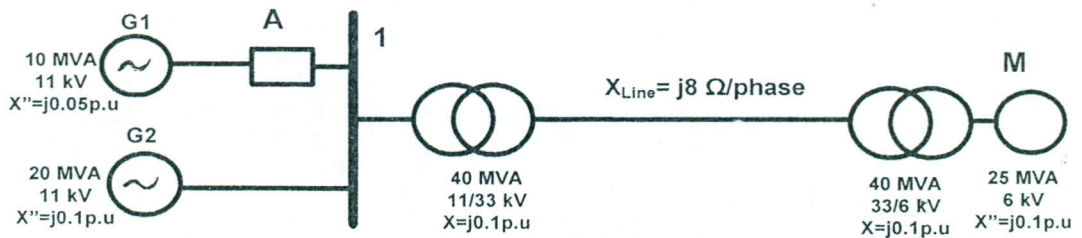


Fig.2

Question # 3: (15 Mark)

A Y-connected solid earthed voltage source with unbalanced voltage $V_{an} = 277\angle 0^\circ$, $V_{bn} = 260\angle -120^\circ$, and $V_{cn} = 295\angle 115^\circ$ V. The source is connected to a Δ - balanced load through a line. The line impedance is $1\angle 83^\circ \Omega$ /phase and phase impedance of Δ -connected load is $30\angle 40^\circ \Omega$.

- Calculate symmetrical components of the source voltages.
- Draw the sequence networks.
- Determine the source currents I_a , I_b , and I_c using the method of symmetrical components.

Question # 4: (20 Mark)

The equipment ratings and per-unit reactances for the power system shown in figure (3) are as follows:

G1: 50 MVA, 11 kV, $X_1=X_2=0.25$, $X_0=0.08$ p.u.

G2: 30 MVA, 11 kV, $X_1=X_2=0.2$, $X_0=0.05$ p.u.

T1: 50MVA, 11/220 kV, $X=0.1$ p.u.

T2: 30 MVA, 11/220 kV, $X=0.08$ p.u.

Line (L): $X_1=X_2=180$ ohms/phase, $X_0=550$ ohms/phase.

The system operates at rated values and a single line to ground fault occurs at bus 1 through fault impedance $Z_f = j15 \Omega$, find:

- Fault current.
- Voltage of bus 1 (a, b, c).
- Current supplied by G1 during a fault.

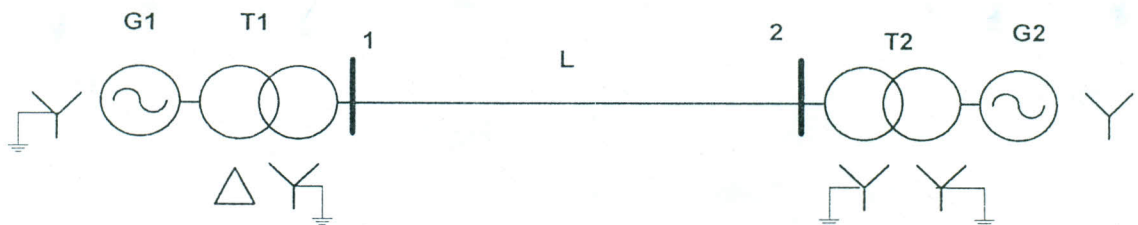


Fig.3

With My Best Wishes
Prof. Dr. Mohammed El-Saied