


10



| | | |
|--|---|---|
| University : Menoufia Faculty : Electronic Engineering Department : Comp. Science & Eng. Academic level : Prep. Year, 1 st term Course Name : Logic Design Course Code : CSE 324 |  | Date : 6/1/2019 Time : 3 Hours No. of pages : 2 Full Mark : 60 Marks Exam : First term Final Exam Examiner : Dr. Ahmed Shehata Part II |
|--|---|---|

(Part II) إبدأ إجابة هذا الجزء من اليمين

Answer the following questions

Question number 1:

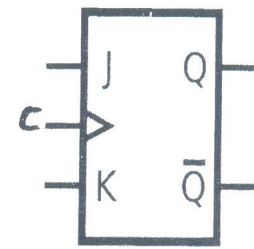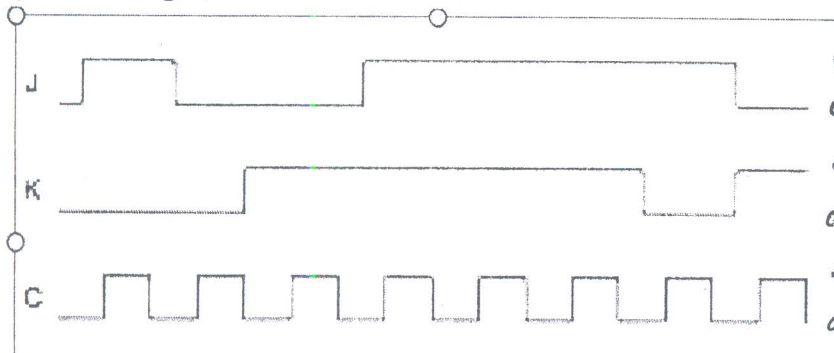- a. According to JK flip Flop and the timing diagram Shown, draw the output Q of the flip flop. Assuming Q=0 at start. (5 Marks)



- b. Construct a 3 to 8 line decoder by using 2-to-4 line decoder, active low output and a single active high enable. (5 Marks)

Question number 2:

- a. Design an asynchronous modulo 6 counter using JK flip flop -ve edge triggered (5 Marks)
- b. Design a counter with T flip-flops that goes through the following binary repeated sequence: 0, 1, 3, 7, 6, 4. Show that when binary states 010 and 101 are considered as don't care conditions. (5 Marks)

Question number 3:

- a. Draw a parallel input serial output 3-bit shift register circuit diagram and implementation. (5 Marks)
- b. Implement a 4-bit bidirectional shift register using a signal that control the shift direction. (5 Marks)

*With my best wishes
Dr. Ahmed Shehata*



(Part I) إبدأ إجابة هذا الجزء من اليسار

1-Answer the following questions:

1-(a) What is the range of signed and unsigned decimal values can be represented using 10 bits?

1-(b) Complete the missing parts

$$(23)_{10} = (\dots)_2 = (\dots)_8 = (\dots)_{16}$$

$$(44.16)_8 = (\dots)_{10} = (\dots)_{16}$$

$$(13)_{10} = (\dots)_{2421} = (\dots)_{Ex-3} = (\dots)_{gray}$$

(10 degree)

2- (a) Perform the following operations in 2's complement system. Use 8 bit (including the sign bit) for each number.

- Add +16 to -18

- Subtract +22 from -18

- Subtract -22 from -18

2- (b) Subtract 17 from 23 using normal subtraction, and 1's complement method

(10 degree)

3-(a) Minimize the following equation using Boolean Algebra

$$X = \overline{(C+D)} + \overline{A} C \overline{D} + A \overline{B} C + \overline{A} \overline{B} C D + A C \overline{D}$$

3-(b) Draw the circuit diagram of the following equation:

$$X = A B C + \overline{A} (B + \overline{C}) + A (B C + \overline{B} \overline{C})$$

Then simplify the above equation using K-Map,

Then draw the circuit diagram of the obtained simplified equation.

(10 degree)

With my best wishes

Prof. Nawal El-Fishawy

مع اطيب تمنياتى بالتوفيق