

University : Menoufia Faculty : Electronic Engineering Department : Electronics & Electrical Communications Academic level : 2 nd Year Course Name : Electronic circuits Course Code : ECE 223		Date : 24/06/2019 Time : 3 Hours No. of pages : 2 Full Mark : 45 Marks Exam : Final Exam Examiner : Dr: A. I. Bahnacy
--	---	--

(برجاء إجابة الجزء الاول من الناحية اليمنى والجزء الثاني من الناحية اليسرى في كراسة الإجابة)

PART 1

Answer all the following questions :

Question No 1 :

(15 Marks)

1-a-What is meant by cross over distortion in class B push-pull amplifier?.

Describe one method to overcome this distortion .

Clarify your answer with drawing.

(7-Marks)

1-b- Find the maximum ac output power, the dc input power and the maximum efficiency of the amplifier shown in Fig. 1. Also determine the input resistance assuming $\beta_{ac}=50$ and $r'_e=6\Omega$.

If the circuit shown in Fig. 1 is replaced by a Darlington class AB push-pull amplifier with $\beta_{ac}=50$ for each transistor, what will be the input resistance?, and , what is the advantage of that? .

(8-Marks)

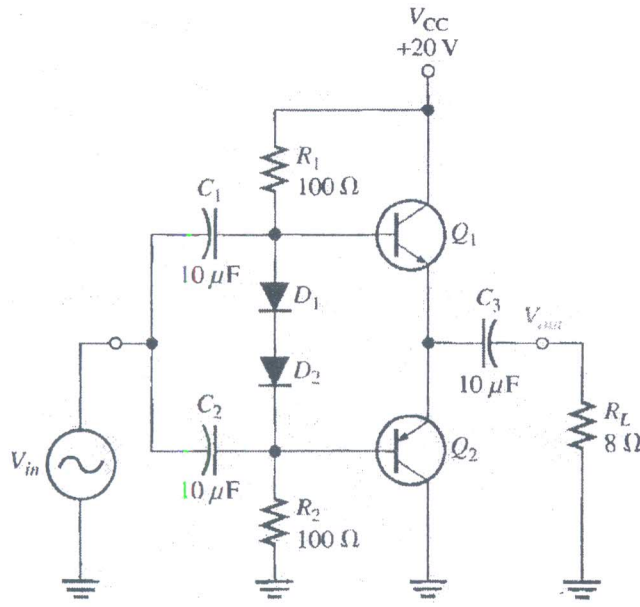


Fig. 1

من فضلك اقلب الورقة

Question No 2:

(15 Marks)

2-a- What is meant by class C amplifier?.

Why application of this amplifier is limited to tuned circuit applications? (3- Marks)

2-b- A certain class C amplifier transistor is ON for 20% of the input cycle. If $V_{ce(sat)}=0.2V$ and $I_{c(sat)}= 25mA$, what is the average power dissipation for maximum output?. Determine the efficiency if $V_{CC}=15V$ and the equivalent parallel resistance in the collector tank circuit is 50Ω . (6-Marks)

2-c- Define: Amplifier frequency response - Dominant critical frequencies - Band width. (6-Marks)

Question No 3 :

(15 Marks)

For the BJT amplifier in Fig. 2 determine:

i- The low critical frequencies of the input, output and bypass RC circuits. (6 Marks)

ii- The high critical frequencies of the input and output RC circuits. (4 Marks)

iii- Draw the Bode plot of the total frequency response and determine the bandwidth.

Consider $\beta_{ac}=125, r'_e=12\Omega, C_{be}=20pF$, and $C_{bc}=2.4pF$. (5 Marks)

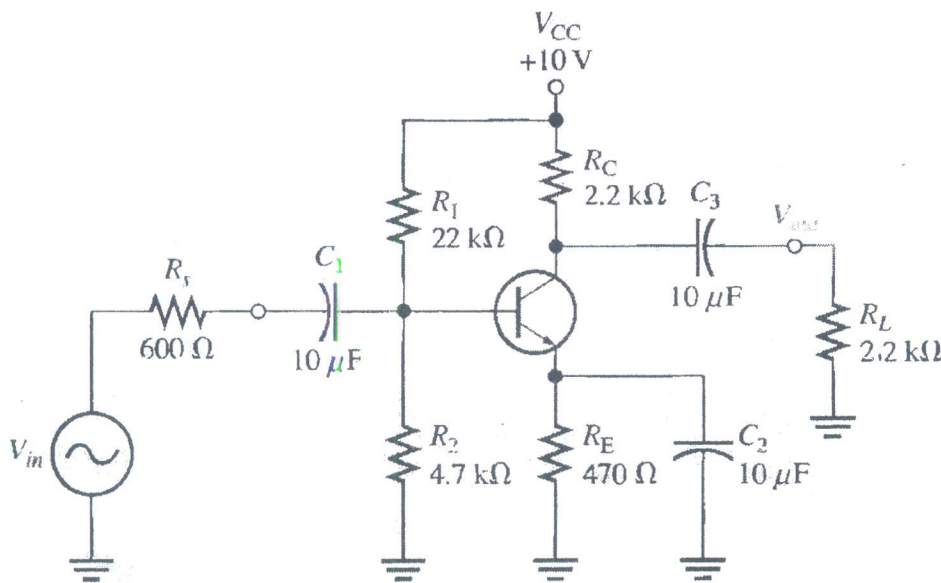


Fig.2

مع أطيب الامنيات بالنجاح والتفوق