

Menoufia University
Faculty of Electronic Eng.
Industrial Elect. and Control Dept.
First Year Exam.



Mid term Exam 2018-2019
Time allowed: 1 hour
Subject: Electrical Meas.
Date: 2/4/2019

الدرجة:


اسم الطالب/الطالبة:

رقم السكشن:

Answer all the following questions

1-a A voltmeter having a full scale deflection of 100V and a sensitivity of $1.6 \text{ k}\Omega/\text{V}$ is used to measure voltage V_1 in the circuit of Figure 1, Determine:

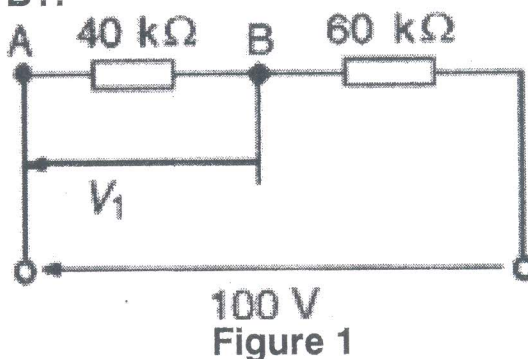- The value of voltage V_1 with the voltmeter is not connected,
- The voltage indicated by the voltmeter when connected between A and B?



1-b Draw and explain briefly each of the following:

- Deadweight pressure gauge.
- Petrol-tank level indicator.

2-a The expected value of the voltage across a resistor is 50V; however, measurements yields a value of 49V. Calculate:

- The absolute error.
- The percent of error.
- The relative accuracy.
- The percent of accuracy.

2-b Explain with the help of sketches each of the following:

- Instrument characteristic with hysteresis.
- Instrument characteristic with dead space.